

FM Detector Notes

Piyush Sud

10/20/2024

1 High Level Design

There are a few different types of fm detectors that are commonly used:

- Foster-Seeley Discriminator
- Ratio Detector
- Quadrature Discriminator

Out of all of these, the Quadrature Discriminator seems to be the best for a few reasons:

- Has a simple design only requiring a few components.
- Does not require an RF transformer, which needs to be weakly coupled in the case of the Foster-Seeley Discriminator - cannot easily find one off of digikey/mouser.
- Works with low input levels and has good linearity.

2 Principle of Operation

The original signal is

$$A\cos(wt)$$


The signal after C2 is shifted by 90 degrees due to the capacitor, and additionally shifted by ϕ due to the difference between the resonant frequency of the tank circuit and the incoming FM signal. Therefore the signal after C2 is

$$A\cos\left(wt + \frac{\pi}{2} + \phi\right)$$

Multiplying these two together gives

$$A\cos(wt) * A\cos\left(wt + \frac{\pi}{2} + \phi\right)$$

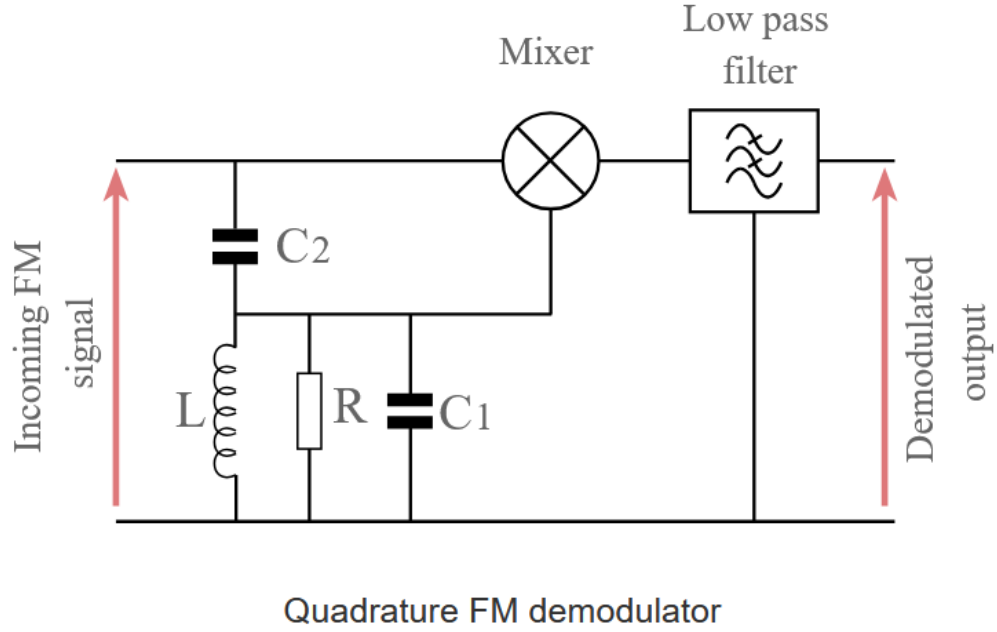By the identity $\cos(a)\cos(b) = \frac{1}{2}[\cos(a-b) + \cos(a+b)]$,



$$= \frac{A^2}{2} \cos(-\pi/2 - \phi) + \cos(2\omega t + \frac{\pi}{2} + \phi)$$

Noting that $\cos(-\pi/2 - \phi) = \sin(\phi)$,

$$= \frac{A^2}{2} \sin(\phi) + \cos(2\omega t + \frac{\pi}{2} + \phi)$$

The higher frequency cosine component can be filtered out, leaving a function whose amplitude is proportional to the phase, which in turn is proportional to $\sin(\phi)$. For small values of ϕ , this is approximately equal to ϕ .

3 Detailed Design

- For the tank circuit, the self resonant frequency is given by $\frac{1}{2\pi\sqrt{LC}}$. If we choose $L = 0.1 \mu\text{H}$, then for a resonant frequency of 10.7 MHz, this gives us 2.21 nF.

4 Mixer Impedance Matching

WAIT AT AUDIO FREQ U CANT USE 0.1 uF BYPASS CAPS! FREQ CAN BE 20 Hz!!


so output needs to be dc coupled to vcc. this won't work. need to choose a different mixer!

The AD831 seems like a good option - it says, "all ports can be DC coupled"!

- For the mixer, at 10.7 MHz the frequency is sufficiently low so we can assume the input impedance is mostly low. In fact, at this frequency PCB trace length is probably not an issue so impedance matching is not necessary.

5 Simulations

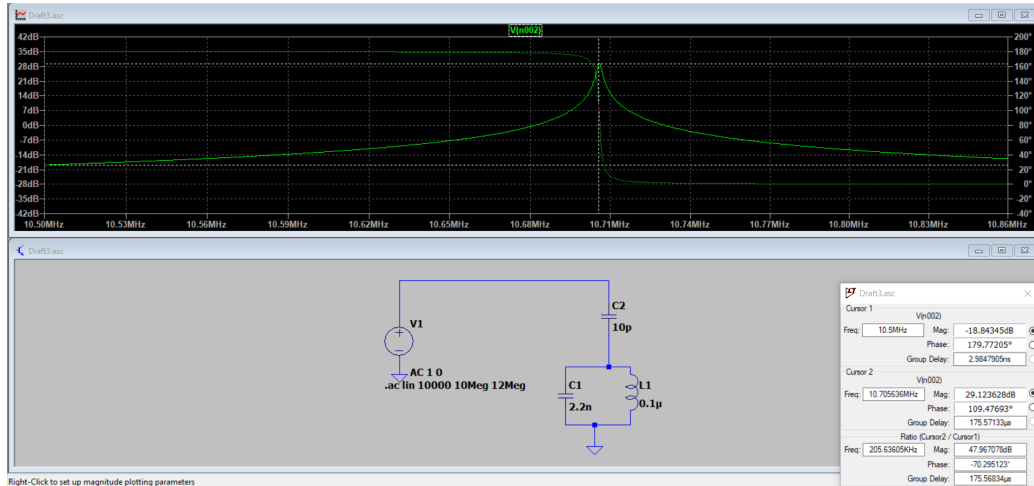Here is a simulation of the tank circuit in the discriminator:



Here's a simulation of the fm detector working at low frequencies (at high frequencies LTSpice doesn't handle it very well)

Here's a simulation of the output impedance:

